

Ohm's Law

Objective: Design a step-by-step experiment procedure to study Ohm's law

Introduction:

Ohm's law states that,


$$V = IR$$

Where V, I, and R represent the voltage in volt, current in ampere, and resistance in ohms, respectively, for a resistor or segment of DC circuit. R is the equivalent resistance if the segment consists of multiple resistors.

Experiment requirement:

Every group will be provided the same equipment as last week including the resistors drawers, a circuit board, cables, and two multimeters.

Build a circuit according to the diagram in figure 1 using resistors with nominal values as $R_1=100\Omega$, $R_2=220\Omega$, $R_3=1k\Omega$, $R_4=2.2k\Omega$, and $R_5=1k\Omega$. A power supply should be connected to points A and B. Vary the voltage setting on power supply from 10 to 20V with at most 1V increment. Choose three different components/segments (at least one from each category in Lists 1 and 2). From these three components/segments, each group member pick one and measure the relevant variables to produce a data table and/or plots to show if the Ohm's law is satisfied (or not).

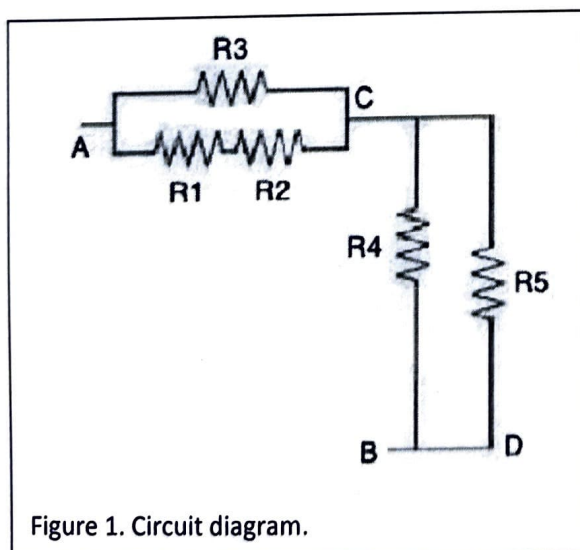

List 1

Components:

R_1 , R_2 , R_3 , R_4 , and R_5

List 2

Circuit segments:

AB, AC, CB

Precaution: pick a dedicated mutlimeter as an ammeter and fix its scale to 200mA. This will avoid a multimeter from switching between ammeter and voltmeter, which can easily blow the fuse. Use the other multimeter when measuring resistance and voltage.

Lab report requirement:

State your procedure clearly. Describe data analysis including uncertainties. Include enough details in your data table(s) and plots. Cite your data and plots to support your conclusion.

Hint:

1. You can use measured R and I to calculate V , then compare it with measured V , or
2. You can fit V vs. I plot with linear function, then compare the slope (should be R) with the measured R .

These are two common approaches, but you are not limited to them. For whichever approach you pick, make sure you understand the uncertainties involved.